

Homework 7: Logical Effort  
ECEn 451  
Dr. David A. Penry

1. Problem 4.8 (remember, drive is the reciprocal of resistance)
2. Problem 4.9
3. Problem 4.10
4. Problem 4.19
5. Problem 4.20