

Homework #4: Pass transistors and design economics  
 ECEn 451  
 Dr. David A. Penry

1. For each of the following circuits, calculate the unknown steady-state voltage assuming that there is a path of “on” transistors through the circuit initially. Assume  $V_{tn}$  is 0.4 V and  $V_{tp}$  is -0.5V:



